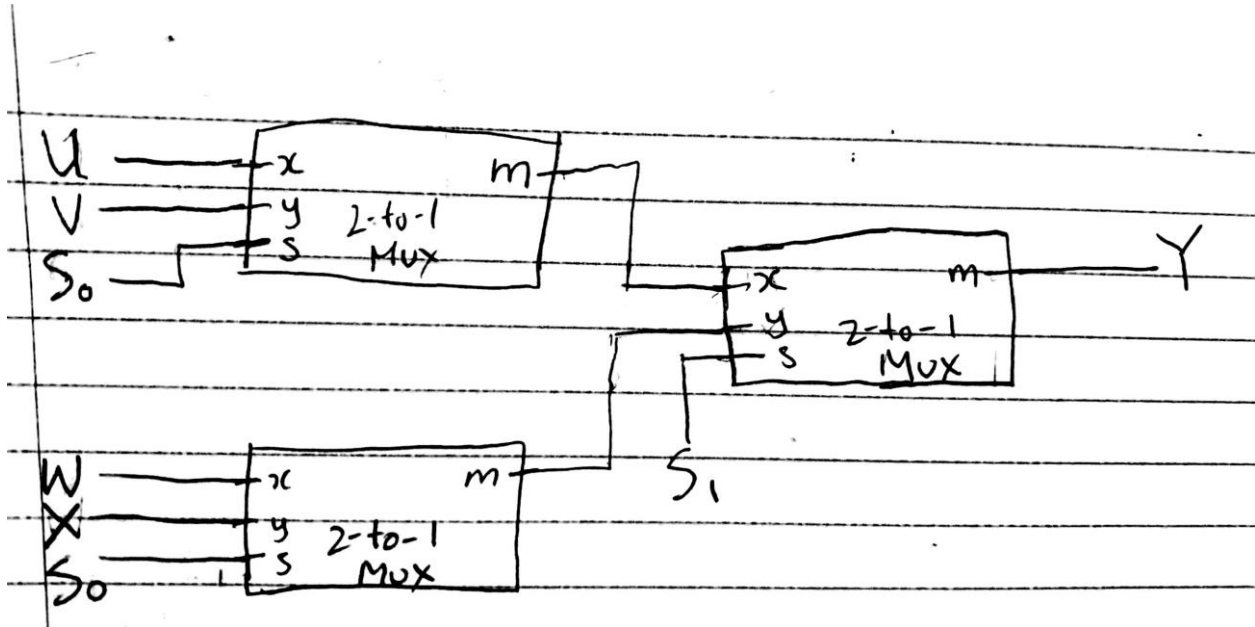



CSC258 Prelab (Lab 2)

Part 2: 4-to-1 Multiplexer

1. The full truth table for the 4-to-1 multiplexer would have 2^6 or 64 rows because there are 6 inputs.
2. Schematic of connecting mux2to1 components to build a 4-to-1 multiplexer:



5. Below is a screenshot of a map of my Logisim design of the 4-to-1 Mux onto a DE1-SoC board

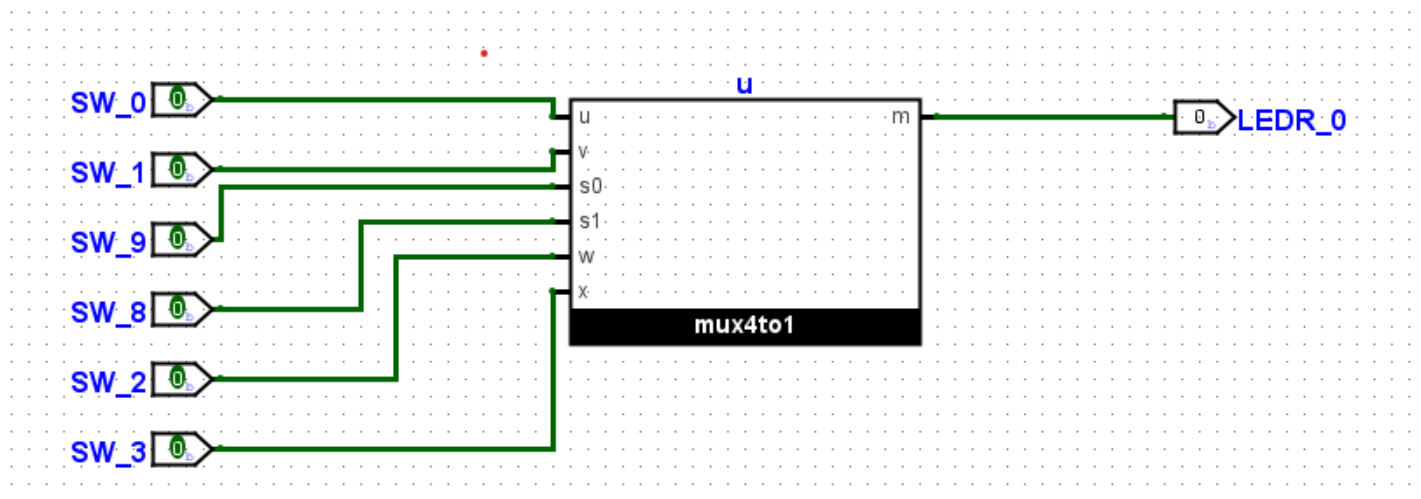

Part 3: 7 Segment Decoder

1. Below is the truth table for each of the 7 segments in the decoder with the Karnaugh maps that correspond to each segment which optimize the Boolean expression for each segment.

A	B	C	D	Segment0	Segment1	Segment2	Segment3	Segment4	Segment5	Segment6
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	0	0	1	1
1	0	1	0	1	1	1	0	1	1	1
1	0	1	1	0	0	1	1	1	1	1
1	1	0	0	1	0	0	1	1	1	0
1	1	0	1	0	1	1	1	1	0	1
1	1	1	0	1	0	0	1	1	1	1
1	1	1	1	1	0	0	0	1	1	1

Segment 0

	CD	CD	CD	CD
AB	1	0	1	1
AB	0	1	1	0
AB	1	0	1	1
AB	0	1	0	1

Boolean Expression: $\overline{B}\overline{D} + \overline{A}C + BC + \overline{A}\overline{D} + \overline{A}B\overline{C} = Y$

Segment 1

	CD	CD	CD	CD
AB	0	1	0	1
AB	1	0	1	0
AB	0	1	0	0
AB	1	0	0	1

Boolean Expression: $\overline{A}B + \overline{B}\overline{D} + \overline{A}C\overline{D} + \overline{A}C\overline{D} + \overline{A}C\overline{D} = Y$

Segment 2

	CD	CD	CD	CD
AB	1	1	1	0
AB	1	1	1	1
AB	0	1	0	0
AB	1	1	1	1

Boolean Expression: $\overline{A}C + \overline{A}D + \overline{C}D + \overline{A}B + \overline{A}B = Y$

Segment 3

	CD	CD	CD	CD
AB	1	0	1	1
AB	0	1	0	1
AB	1	1	0	1
AB	1	0	1	0

Boolean Expression: $\overline{A}B\overline{D} + \overline{B}C\overline{D} + \overline{B}C\overline{D} + \overline{B}C\overline{D} + \overline{A}C\overline{D} = Y$

Segment 4

	CD	CD	CD	CD
AB	1	0	0	1
AB	0	0	0	1
AB	1	1	1	1
AB	1	0	1	1

Boolean Expression: $\overline{B}\overline{D} + \overline{C}\overline{D} + \overline{A}C + \overline{A}B = Y$

Segment 5

	CD	CD	CD	CD
AB	1	0	0	0
AB	1	0	0	1
AB	1	0	1	1
AB	1	1	1	1

Boolean Expression: $\overline{C}\overline{D} + \overline{A}B + \overline{B}\overline{D} + \overline{A}C + \overline{A}B\overline{C} = Y$

Segment 6

	CD	CD	CD	CD
AB	0	0	1	1
AB	1	1	0	1
AB	0	1	1	1
AB	1	1	1	1

Boolean Expression: $\overline{B}C + \overline{C}\overline{D} + \overline{A}B + \overline{A}D + \overline{A}B\overline{C} = Y$

3. Below are the screenshots of the test vectors for each segment of the decoder.

Segment 0:

Passed: 16 Failed: 0					
status	A	B	C	D	Y
pass	0	0	0	0	1
pass	0	0	0	1	0
pass	0	0	1	0	1
pass	0	0	1	1	1
pass	0	1	0	0	0
pass	0	1	0	1	1
pass	0	1	1	0	1
pass	0	1	1	1	1
pass	1	0	0	0	1
pass	1	0	0	1	1
pass	1	0	1	0	1
pass	1	0	1	1	0
pass	1	1	0	0	1
pass	1	1	0	1	0
pass	1	1	1	0	1
pass	1	1	1	1	1

Segment 1:

Passed: 16 Failed: 0					
status	A	B	C	D	Y
pass	0	0	0	0	1
pass	0	0	0	1	1
pass	0	0	1	0	1
pass	0	0	1	1	1
pass	0	1	0	0	1
pass	0	1	0	1	0
pass	0	1	1	0	0
pass	0	1	1	1	1
pass	1	0	0	0	1
pass	1	0	0	1	1
pass	1	0	1	0	1
pass	1	0	1	1	0
pass	1	1	0	0	0
pass	1	1	0	1	1
pass	1	1	1	0	0
pass	1	1	1	1	0

Segment 2:

Passed: 16 Failed: 0					
status	A	B	C	D	Y
pass	0	0	0	0	1
pass	0	0	0	1	1
pass	0	0	1	0	0
pass	0	0	1	1	1
pass	0	1	0	0	1
pass	0	1	0	1	1
pass	0	1	1	0	1
pass	0	1	1	1	1
pass	1	0	0	0	1
pass	1	0	0	1	1
pass	1	0	1	0	1
pass	1	0	1	1	1
pass	1	1	0	0	0
pass	1	1	0	1	1
pass	1	1	1	0	0
pass	1	1	1	1	0

Segment 3:

Passed: 16 Failed: 0					
status	A	B	C	D	Y
pass	0	0	0	0	1
pass	0	0	0	1	0
pass	0	0	1	0	1
pass	0	0	1	1	1
pass	0	1	0	0	0
pass	0	1	0	1	1
pass	0	1	1	0	1
pass	0	1	1	1	0
pass	1	0	0	0	1
pass	1	0	0	1	0
pass	1	0	1	0	0
pass	1	0	1	1	1
pass	1	1	0	0	1
pass	1	1	0	1	1
pass	1	1	1	0	1
pass	1	1	1	1	0

Segment 4:

Passed: 16 Failed: 0					
status	A	B	C	D	Y
pass	0	0	0	0	1
pass	0	0	0	1	0
pass	0	0	1	0	1
pass	0	0	1	1	0
pass	0	1	0	0	0
pass	0	1	0	1	0
pass	0	1	1	0	1
pass	0	1	1	1	0
pass	1	0	0	0	1
pass	1	0	0	1	0
pass	1	0	1	0	1
pass	1	0	1	1	1
pass	1	1	0	0	1
pass	1	1	0	1	1
pass	1	1	1	0	1
pass	1	1	1	1	1

Segment 5:

Passed: 16 Failed: 0					
status	A	B	C	D	Y
pass	0	0	0	0	1
pass	0	0	0	1	0
pass	0	0	1	0	0
pass	0	0	1	1	0
pass	0	1	0	0	1
pass	0	1	0	1	1
pass	0	1	1	0	1
pass	0	1	1	1	0
pass	1	0	0	0	1
pass	1	0	0	1	1
pass	1	0	1	0	1
pass	1	0	1	1	1
pass	1	1	0	0	1
pass	1	1	0	1	0
pass	1	1	1	0	1
pass	1	1	1	1	1

Segment 6:

Passed: 16 Failed: 0					
status	A	B	C	D	Y
pass	0	0	0	0	0
pass	0	0	0	1	0
pass	0	0	1	0	1
pass	0	0	1	1	1
pass	0	1	0	0	1
pass	0	1	0	1	1
pass	0	1	1	0	1
pass	0	1	1	1	0
pass	1	0	0	0	1
pass	1	0	0	1	1
pass	1	0	1	0	1
pass	1	0	1	1	1
pass	1	1	0	0	0
pass	1	1	0	1	1
pass	1	1	1	0	1
pass	1	1	1	1	1