 


# CSC258 Prelab (Lab 1)

## Part 1: 2-to-1 Multiplexer

1. Using only the AND, OR and NOT gates, below is a circuit with input  $y$ ,  $s$  and  $x$  and output  $f=xs'+ys$ .




2. Below is the truth table of  $xs'+ys$ .

$X$	$Y$	$S$	$XS'+YS$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

## Part 2:

 1. Below is a circuit implementation of  $f = (a + b)' + cb'$ .



2. Below is the truth table of  $(a + b)' + cb'$ .

A	B	C	$(A+B)' + CB'$
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

3. There is a cheaper implementation for the design. The Boolean expression above required 5 gates as shown in the circuit diagram. Using the following operations, we can show that only 4 gates are required.

$$\begin{aligned}
 & (a + b)' + cb' \\
 &= a'b' + cb' \text{ (DeMorgan's Law)} \\
 &= b'(a' + c) \text{ (Distributive Law)}
 \end{aligned}$$

We see that  $b'(a' + c)$  is an equivalent Boolean expression compared to  $(a + b)' + cb'$  and only requires 4 gates to implement as a circuit.

Below is the cheaper implementation of the circuit in step 1.

